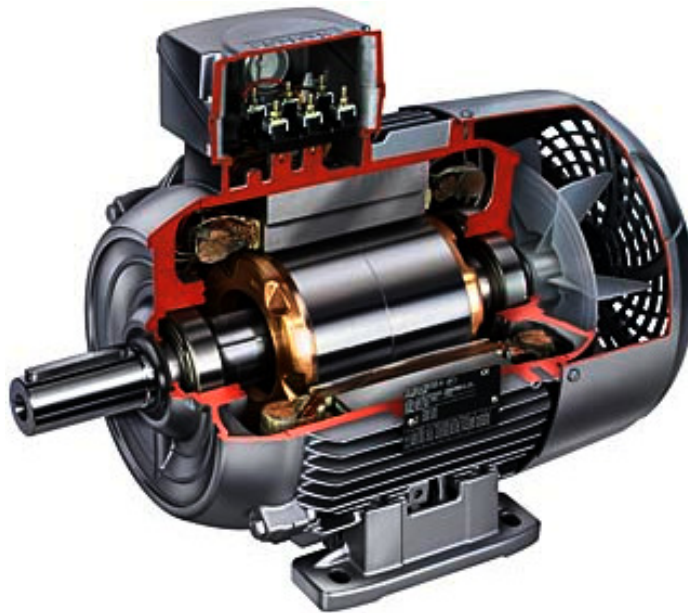
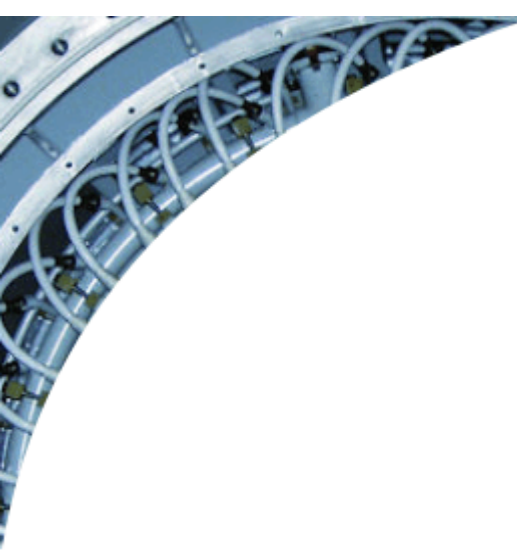


EEE 3352

Electromechanics & Electrical Machines

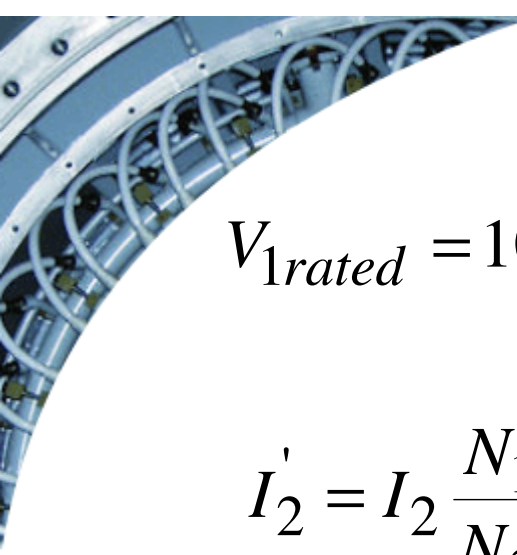


Lecture 4: Examples



Example 4.1:

- A 220/100-V transformer has a total resistance of $2\ \Omega$ and a total leakage reactance of $3\ \Omega$ both referred to the primary.
- The secondary current is 10 A.


$$V_{1rated} = 100 \text{ V}, V_{2rated} = 220 \text{ V}, R_T = 2 \text{ } \Omega, X_T = 3 \text{ } \Omega, I_2 = 10 \text{ A}$$

$$I_2' = I_2 \frac{N_1}{N_2} = 10 \times \frac{100}{220} = 4.5 \text{ A}$$

$$Z_T = \sqrt{R_T'^2 + X_T'^2} = \sqrt{2^2 + 3^2} = 3.6 \text{ } \Omega$$

$$\phi_T = \tan^{-1} \frac{X_T}{R_T} = \tan^{-1} \frac{3}{2} = 56.3^\circ$$

$$\text{Reg} = \frac{I_2' Z_T}{V_1} \cos(\phi_T - \phi_L)$$

- 
- Find the regulation at zero power factor lag

$$\phi_L = 90^\circ$$

$$\text{Reg} = \frac{I'_2 Z_T}{V_1} \cos(\phi_T - \phi_L)$$

$$\text{Reg} = \frac{4.5 \times 3.6}{220} \cos(56.3^\circ - 90^\circ) = \underline{\underline{0.061}}$$

- 
- Find the regulation at unity power factor

$$\phi_L = 0^\circ$$

$$\text{Reg} = \frac{I'_2 Z_T}{V_1} \cos(\phi_T - \phi_L)$$

$$\text{Reg} = \frac{4.5 \times 3.6}{220} \cos(56.3^\circ - 0^\circ) = \underline{\underline{0.041}}$$

- 
- Find the regulation at zero power factor lead

$$\phi_L = -90^\circ$$

$$\text{Reg} = \frac{I'_2 Z_T}{V_1} \cos(\phi_T - \phi_L)$$

$$\text{Reg} = \frac{4.5 \times 3.6}{220} \cos(56.3^\circ - (-90^\circ)) = \underline{\underline{-0.061}}$$

- 
- Find the power factor which gives maximum regulation

$$\phi_L = \phi_T = 56.3^\circ$$

$$\text{p.f.} = \cos \phi_L = \cos 56.3^\circ = \underline{\underline{0.56 \text{ lag}}}$$

- 
- Find the maximum regulation

$$\text{Reg}_{\max} = \frac{I'_2 Z_T}{V_1}$$


$$\text{Reg}_{\max} = \frac{4.5 \times 3.6}{220} = \underline{\underline{0.0736}}$$

- 
- Find the power factor which gives zero regulation

$$\phi_L - \phi_T = 90^\circ$$

$$\phi_L = 90^\circ + \phi_T = 90^\circ + 56.3^\circ$$

$$\text{p.f.} = \cos \phi_L = \cos 146.3^\circ = \underline{\underline{-0.832}} \text{ or } \underline{\underline{0.832 \text{ lead}}}$$

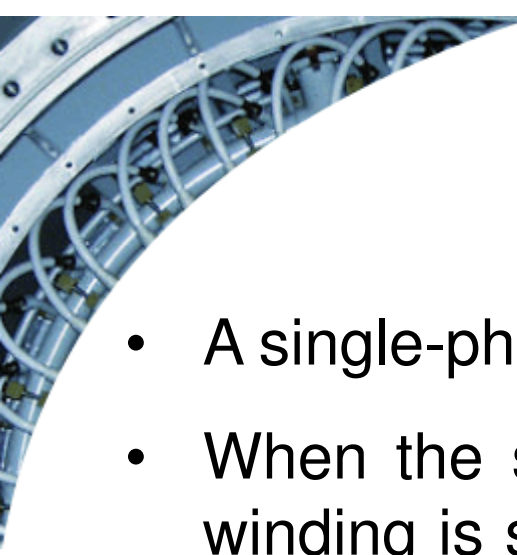

Example 4.2

- A single-phase transformer is rated at 10 kVA, 240/100 V
- When the secondary terminals are open-circuited and the primary winding is supplied at normal voltage, the input current is 2.6 A at a power factor of 0.3 lag

$$V_{1rated} = 240 \text{ V}, V_{2rated} = 100 \text{ V}, S_{rated} = 10 \text{ kVA}$$

$$V_1 = 240 \angle 0^\circ \text{ V}$$


$$\theta_o = \cos^{-1} 0.3 = 72.5^\circ$$

Open circuit

$$I_2 = 0 = I_2'$$


$$|I_1| = |I_o| = 2.6 \text{ A}$$

$$I_o = 2.6 \angle -72.5^\circ \text{ A} = 0.78 - j2.48 \text{ A} = |I_{Loss}| + j|I_{mag}|$$

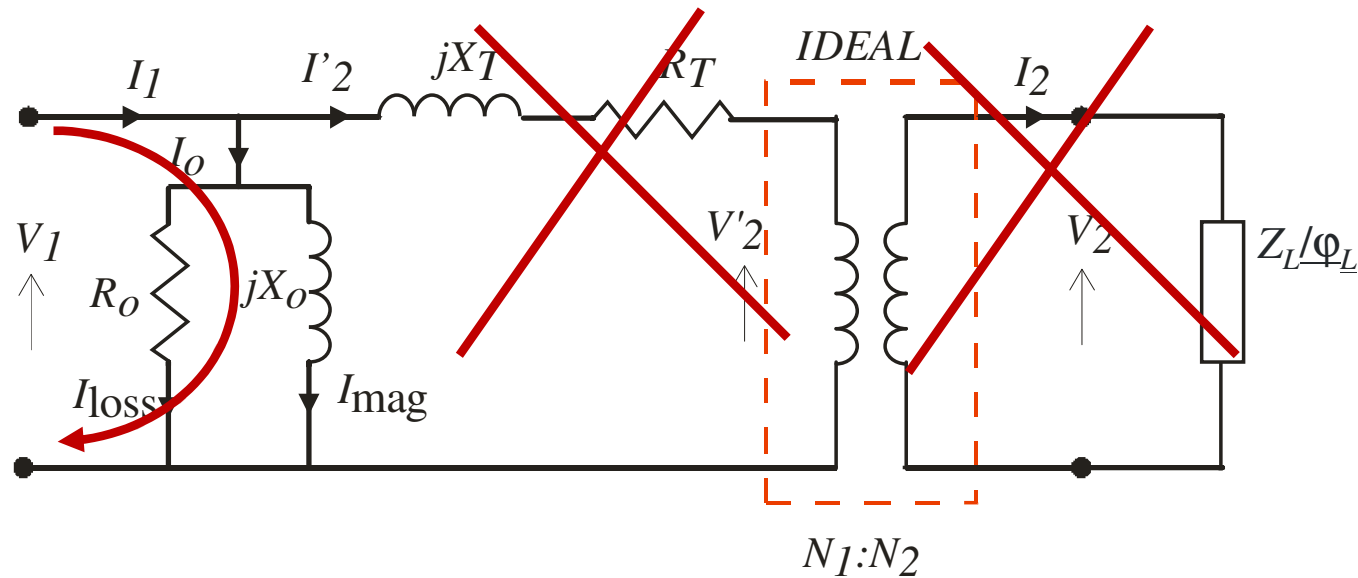

$$R_o = \frac{V_1}{I_{Loss}} = \frac{240}{0.78} = 308 \, \Omega$$

$$X_o = \frac{V_1}{I_{mag}} = \frac{240}{2.48} = 97 \, \Omega$$

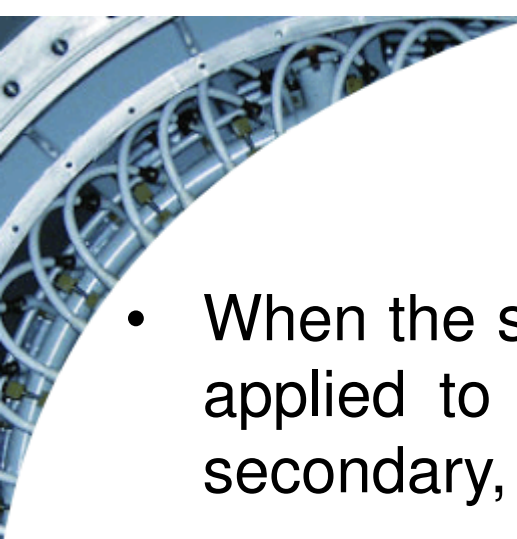
- 
- When the secondary terminals are short-circuited, a voltage of 18 V applied to the primary causes the full-load current to flow in the secondary, the power input to the primary being 240 W.

$$V_1 = 18\angle 0^\circ \text{ V}$$

$$P_1 = 240 \text{ W}$$

$$I_1 = I_{FL} = \frac{S_r}{V_{1rated}} = \frac{10 \times 10^3}{240} = 41.7 \text{ A}$$


Short circuit

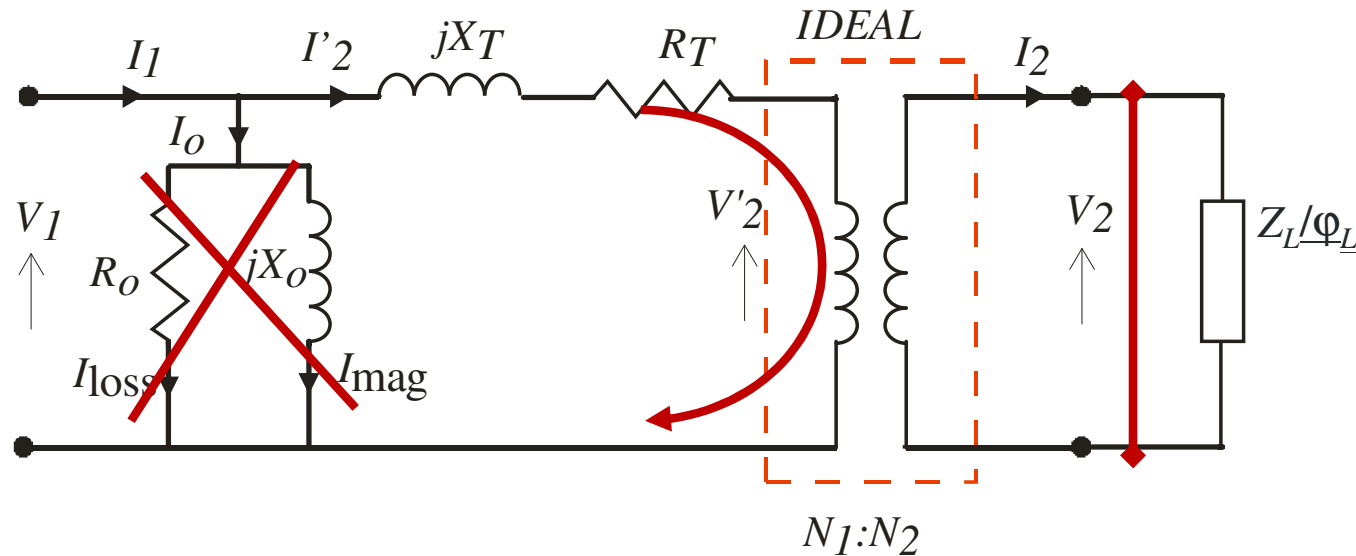

$$I_1^2 R_T = P \rightarrow R_T = \frac{P}{I_1^2} = \frac{240}{41.7^2} = 0.14 \, \Omega$$

$$Z_T = \frac{V_1}{I_1} = \frac{18}{41.7} = 0.43 \, \Omega$$

$$Z_T^2 = R_T^2 + X_T^2 \rightarrow X_T = \sqrt{Z_T^2 - R_T^2} = \sqrt{0.43^2 - 0.14^2} = 0.41 \, \Omega$$

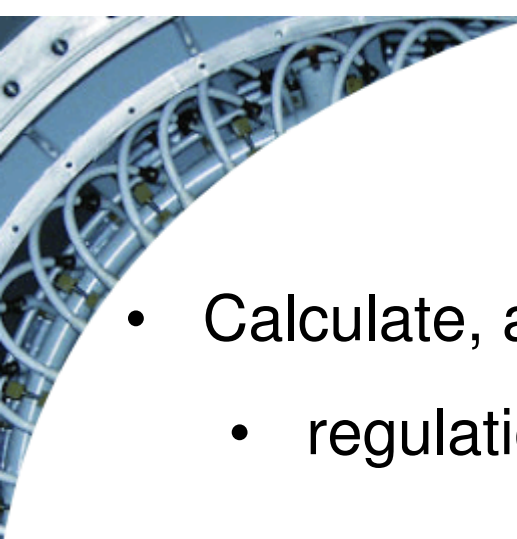
- 
- Calculate, at full load unity power factor, the:
 - regulation


$$\text{Reg} = \frac{I'_2 Z_T}{V_1} \cos(\phi_T - \phi_L)$$

$$I_{2FL} = I_{2rated} = \frac{S_r}{V_{2r}} = \frac{10 \times 10^3}{100} = 100 \text{ A}$$

$$I'_2 = \frac{N_2}{N_1} I_2 = \frac{100}{240} \times 100 = 41.7 \text{ A}$$

$$Z_T = 0.43 \, \Omega \quad \left| \quad \phi_T = \tan^{-1} \frac{X_T}{R_T} = \tan^{-1} \frac{0.41}{0.14} = 71.1^\circ \quad \left| \quad \phi_L = 0^\circ\right.$$

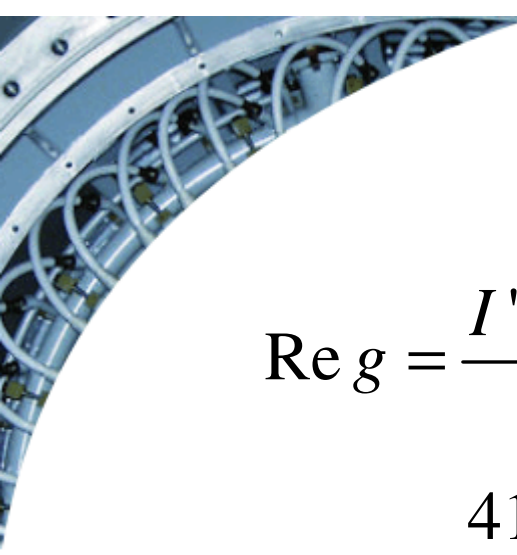
$$\begin{aligned}\text{Re } g &= \frac{I'_2 Z_T}{V_1} \cos(\phi_T - \phi_L) \\ &= \frac{41.7 \times 0.43}{240} \cos(71.1^\circ - 0^\circ) \\ &= 0.024 \\ &= \underline{\underline{2.4\%}}\end{aligned}$$

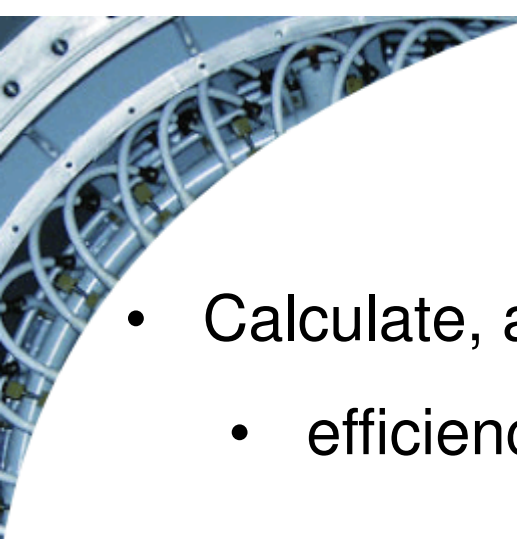- 
- Calculate, at full load unity power factor, the:
 - efficiency


$$\eta = \frac{x S_r \cos \phi_L}{x S_r \cos \phi_L + P_{Fe} + x^2 P_{CuFL}}$$

$$x = 1$$

P_{CuFL} = power at full-load short circuit power = 240 W

or $P_{CuFL} = I_{2FL}^2 R_T = 41.7^2 \times 0.14 = 243 \text{ W}$ (round off error in R_T)

P_{Fe} = power at no-load with open circuit voltage
 $= V_1 I_o \times \text{p.f.} = 240 \times 2.6 \times 0.3 = 187.2 \text{ W}$

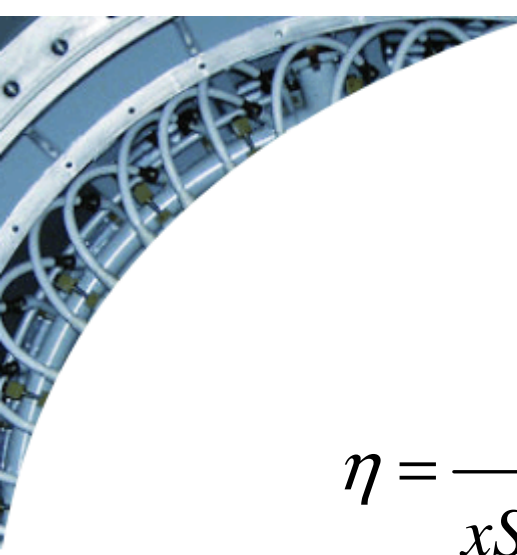
$$\begin{aligned}\eta &= \frac{xS_r \cos \phi_L}{xS_r \cos \phi_L + P_{Fe} + x^2 P_{CuFL}} \\ &= \frac{1 \times (10 \times 10^3) \times 1}{1 \times (10 \times 10^3) \times 1 + 187.2 + 1^2 \times 240} \\ &= 0.959 \\ &= \underline{\underline{95.9\%}}\end{aligned}$$