
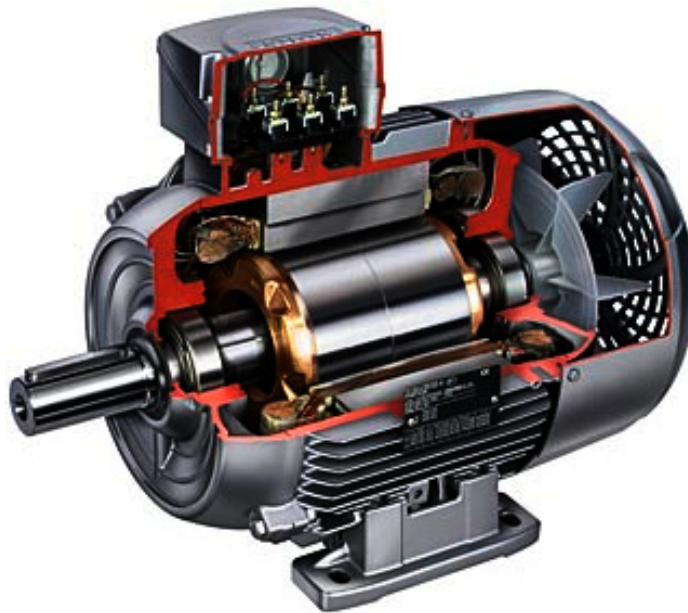


EEE 3352

Electromechanics & Electrical Machines

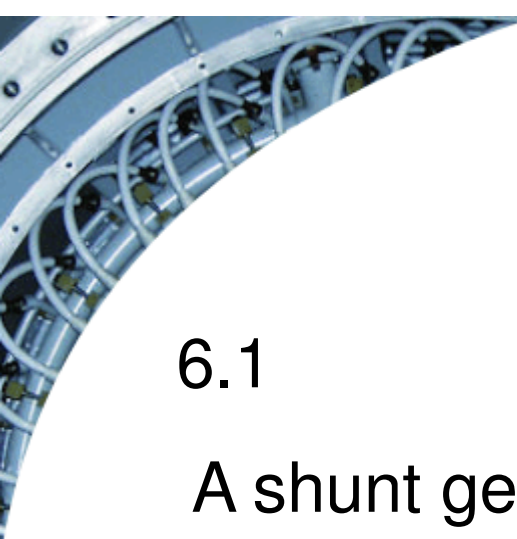

Lecture 6: Examples



Examples:

6.1

A shunt generator has a field resistance of $60\ \Omega$. When the generator delivers $6\ \text{kW}$, the terminal voltage is $120\ \text{V}$, while the generated EMF is $133\ \text{V}$. Determine the

(a) armature circuit resistance and


(b) EMF when the output is $2\ \text{kW}$ and terminal voltage is $135\ \text{V}$

$$R_f = 60 \Omega$$

$$P = 6 \text{ kW}$$

$$V_a = 120 \text{ V}$$

$$V_{in} = 133 \text{ V}$$

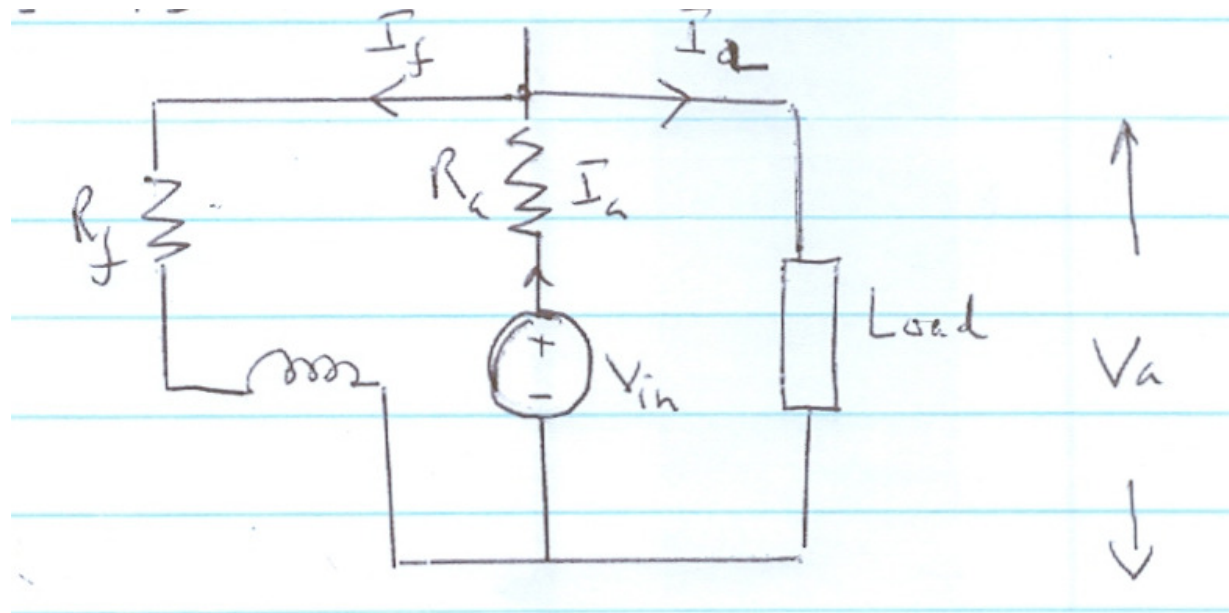

(a)

$$\bar{I}_L = \frac{P}{V_a} = \frac{6 \times 10^3}{120} = 50 \text{ A}$$

$$\bar{I}_f = \frac{V_a}{R_f} = \frac{120}{60} = 2 \text{ A}$$

$$\bar{I}_a = \bar{I}_f + \bar{I}_L = 50 + 2 = 52 \text{ A}$$

$$R_a = \frac{V_{in} - V_a}{\bar{I}_a} = \frac{133 - 120}{52} = \underline{\underline{0.25 \Omega}}$$

(b)


$$V_a = 135 \text{ V} \quad ; \quad P_L = 2 \text{ kW}$$

$$I_L = \frac{2 \times 10^3}{135} = 14.4 \text{ A}$$

$$I_f = \frac{135}{60} = 2.25 \text{ A}$$

$$I_a = I_f + I_L = 17.15 \text{ A}$$
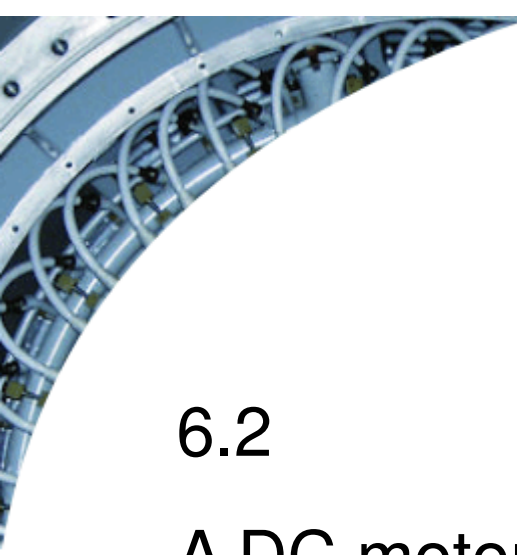
$$V_{in} = V_a + I_a R_a = 135 + 17.15 \times 0.25 \text{ A} = \underline{\underline{139.3 \text{ V}}}$$



6.2

A DC motor operates at **1680 r/min** when drawing **28 A** from a **230-V** supply. If the armature resistance is **0.25 Ω** , and assuming all losses are neglected, calculate the


- (a) no-load speed
- (b) developed power under loaded conditions
- (c) torque developed under the given load

$$n = 1680 \text{ r/min}$$

$$I_a = 28 \text{ A}$$

$$V_s = 230 \text{ V}$$

$$R_a = 0.25 \Omega$$

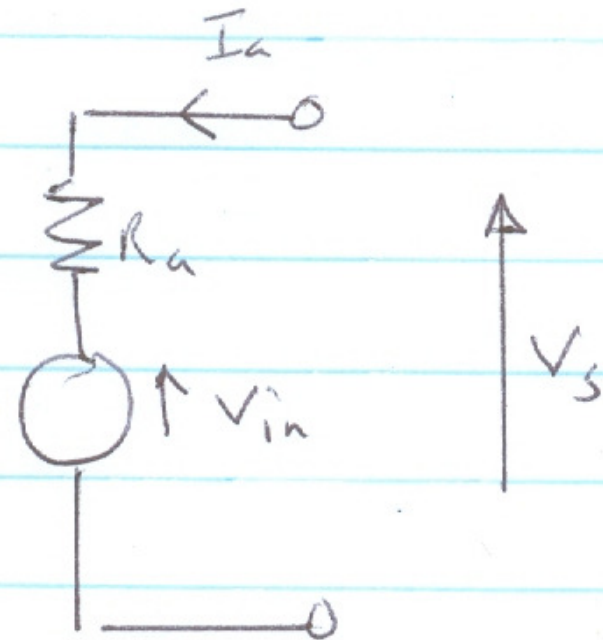

Assume :

- Separately excited
- ϕ is constant.

(a)

$$I_L = I_{a1} = 28A \quad ; \quad n_1 = 1680 \text{ r/min}$$

$$V_{in1} = V_a - I_{a1} R_a = 230 - 28 \times 0.25 = 223 \text{ V}$$

$$V_{in1} = k \omega \phi = 1680 k \phi \Rightarrow k \phi = \frac{223}{1680} = 0.1327$$

At no-load, $I_{a2} = 0$, $V_{in2} = V_a = 230 \text{ V}$

$$V_{in2} = k \omega n_2 \Rightarrow 230 = k \phi n_2$$

$$n_2 = \frac{230}{0.1327} = \underline{\underline{1733 \text{ r/min}}}$$


(b)

$$P = V_{in} I_n = 223 \times 28 = 6244 \text{ W}$$

(c)

$$P = \omega T = 2\pi n T$$
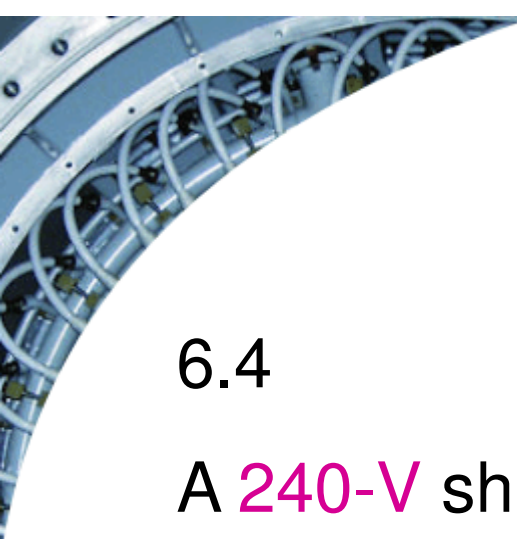
$$T = P / 2\pi n = \frac{6244}{2\pi (1680/60)} = \underline{\underline{35.5 \text{ Nm}}}$$



6.4

A 240-V shunt motor runs at 800 r/min when the armature current at no-load

the armature and field circuit resistance are 0.4 and 160 Ω , respectively

calculate the required resistance to be placed in series with the field to increase the speed to 950 r/min when armature current is 20 A

$$V_s = 240 \text{ V}$$

$$n_1 = 800 \text{ r/min}$$

$$n_2 = 950 \text{ r/min}$$


$$\bar{I}_a = 20 \text{ A}$$

$$R_f = 160 \, \Omega$$

$$R_a = 0.4 \, \Omega$$

$$P(\omega + \bar{I} + \bar{I}_c) = 0$$

$$\phi \propto I_f$$

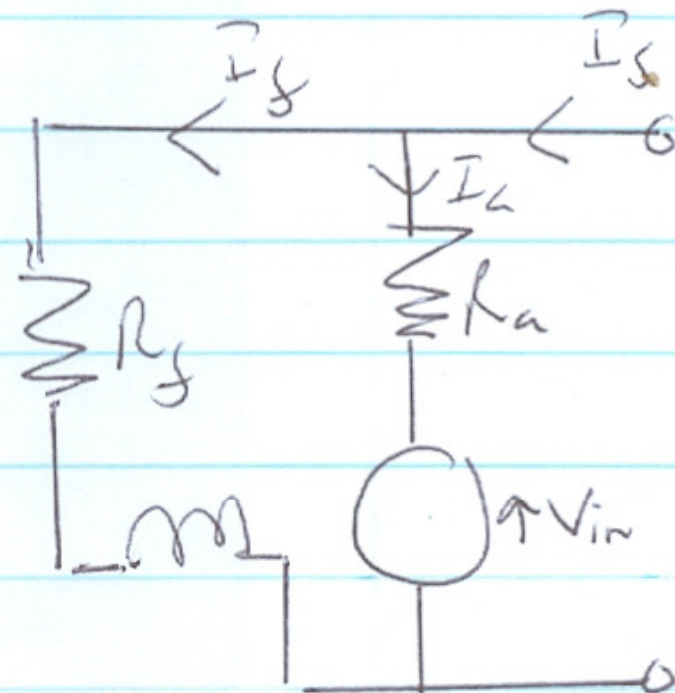

Case 1, no-load, $I_a = 0$

$$V_{in_1} = 240 = k_e n_1 \phi$$

$$k_e \phi_1 = 240 / 800 =$$

$$I_{f_1} = \cancel{240} \frac{V_s}{R_f} = \frac{240}{160} = 1.5 \text{ A}$$

Case 2, new R_f .

$$V_{in2} = V_s - \bar{I}_a R_a = 240 - 20 \times 0.4 = 232$$

$$V_{in2} = k_e \Phi_2 n_2 = k_e \Phi_2 \times 950$$

$$\Phi_2 = \Phi_1 \frac{\bar{I}_{f2}}{\bar{I}_{f1}} \quad \text{or } \text{with}$$

$$232 = k_e \Phi_1 \frac{\bar{I}_{f2}}{\bar{I}_{f1}} \times 950 = \frac{240}{800} \times \frac{\bar{I}_{f2}}{1.5} \times 950$$

$$\bar{I}_{f2} = 1.221 \text{ A}$$

$$R_{ex} + 160 = \frac{240}{1.221} = 197 \Omega$$

$$\underline{\underline{R_{ex} = 37 \Omega}}$$