

[Dashboard](#) / [My courses](#) / [EEE 3352](#) / [Lecture 4: Single phase transformer](#) / [Assignment 4 \(Quiz\): 9 October 2022: 1600-1730 hrs](#)**Started on** Sunday, 9 October 2022, 4:06 PM**State** Finished**Completed on** Sunday, 9 October 2022, 5:14 PM**Time taken** 1 hour 7 mins**Grade** 100.0 out of 100.0

## Question 1

Correct

Mark 10.0 out of 10.0

A 200-kVA, 50-Hz, 1732 / 240-V single-phase transformer has an iron core cross-sectional area of 22500 mm<sup>2</sup>, and the maximum allowable magnetic flux density is 1.4 T. Calculate the number of primary turns  $N_1$ . [Whole number, i.e. 0 decimal places].

Answer: 

The correct answer is: 248

## Question 2

Correct

Mark 5.0 out of 5.0

With the information in Question 1, calculate the number of secondary turns  $N_2$ . [Whole number, i.e. 0 decimal places]

Answer: 

The correct answer is: 34

**Question 3**

Correct

Mark 5.0 out of 5.0

With the information in Question 1, calculate the rated primary current  $I_1$ , in A. [Whole number, i.e. 0 decimal places]

Answer: 

The correct answer is: 115

**Question 4**

Correct

Mark 5.0 out of 5.0

With the information in Question 1, calculate the rated secondary current  $I_2$ , in A. [Whole number, i.e. 0 decimal places]

Answer: 

The correct answer is: 833

**Question 5**

Correct

Mark 10.0 out of 10.0

The length of the magnetic circuit of the transformer given in Question 1 is 4 m and the relative permeability is 2000. What is the magnetising reactance  $X_\phi$ , in  $\Omega$  [Whole number, i.e. 0 decimal places]

Answer: 

The correct answer is: 272

## Question 6

Correct

Mark 5.0 out of 5.0

With information given in the previous questions, what is the magnetising current  $I_{mag}$ , in A? [1 decimal place]

Answer: 

The correct answer is: 6.4

## Question 7

Correct

Mark 10.0 out of 10.0

With the information in Question 1, what is the iron-loss resistance  $R_o$ , in  $\Omega$ , if the iron loss is 2 kW? [Whole number, i.e. 0 decimal places].

Answer: 

The correct answer is: 1500

## Question 8

Correct

Mark 5.0 out of 5.0

With the information in previous questions, what is the iron-loss current  $I_{Loss}$ , in A? [2 decimal places].

Answer: 

The correct answer is: 1.15

**Question 9**

Correct

Mark 10.0 out of 10.0

With the information in previous questions/answers and given that the load current  $I_2$  is 200 A at 0.8 power factor lag, what is the supply current  $I_1$ , in A? [1 decimal place].

Answer: 

The correct answer is: 32.7

**Question 10**

Correct

Mark 5.0 out of 5.0

A 10-MVA transformer has iron losses of 72 kW and full-load copper losses of 200 kW. At what load current  $x$ , a pure number, does maximum efficiency occur? [1 decimal place]

Answer: 

The correct answer is: 0.6

**Question 11**

Correct

Mark 10.0 out of 10.0

A 10-MVA transformer has iron losses of 72 kW and full-load copper losses of 200 kW. What is the maximum efficiency,  $\eta_{max}$ , a pure number? [2 decimal places].

Answer: 

The correct answer is: 0.98

**Question 12**

Correct

Mark 15.0 out of 15.0

A 240-V / 110-V transformer has a total resistance of  $2\ \Omega$  and a total leakage reactance of  $4\ \Omega$ , both referred to the primary-side. The secondary current is 12 A. What is the regulation at unity power factor? [2 decimal places]

Answer: 

The correct answer is: 0.05

**Question 13**

Correct

Mark 5.0 out of 5.0

With the information in Question 12, what is the power factor, a pure number, which gives maximum regulation? [2 decimal places]

Answer: 

The correct answer is: 0.45

[◀ \[2021\] LECTURE 4 - EXAMPLES](#)[\[2021\] LECTURE 5: ROTATING MACHINES ►](#)