EEE 3121 - Signals & Systems

Lecture 5: System Analysis I

Instructor: Jerry MUWAMBA Email: jerry.muwamba@unza.zm jerrymuwamba@yahoo.com

March/April 2021

University of Zambia School of Engineering, Department of Electrical & Electronic Engineering

References

Our main reference text book in this course is

- B. P. Lathi and R. A. Green, Linear Systems and Signals, 3rd Ed., 2018, Oxford University Press, New York. ISBN 978-0-19-020017-6
- [2] Kuo Franklin, F., Network Analysis and Synthesis, 3rd Ed., 1986, J. Wiley (SE), ISBN 0-471-51118-8.
- [3] Sundararanjan, D., A Practical Approach to Signals and Systems, 2008, John Wiley & Sons (Asia) Pte Ltd, ISBN 978-0-470-82353-8.

However, feel free to use pretty much any additional text which you might find relevant to our course.

5.1 Introduction

- □ Here we apply our knowledge of differential equations to analyse Linear Time-Invariant continuous-time (LTIC) systems.
 - Typically at time t = 0 a switch is closed which connects an energy source (voltage or current) source to a system as shown in Fig. 5.1.
 - **This is analogous with applying the energy signal** s(t) = e(t)u(t).
- Before the switch is closed, the currents and voltages in the systems have known values (initial conditions) at t = 0 .
- Thus, we need the initial conditions just after the switch closes at t = 0 +, to solve the network equations



Fig. 5.1: Switching action

5.1 Introduction Cont'd

■ By the superposition principle, the current through any element in a linear circuit with *n* voltage and *m* current sources is equal to the algebraic sum of currents through the same element resulting from the sources taken one at a time, the other sources having been suppressed.



Fig. 5.2*a*

- □ For the LTI system in Fig. 5.2*a*, to find the current $i_T(t)$ through an element *Z* shown:
- ❑ We open-circuit all current sources and short-circuit n 1 voltage sources, to leave only v_j(t), see Fig. 5.2b.
 ❑ Let i (t) denote the current

□ Let $i_{v_j}(t)$ denote the current through Z due to $v_i(t)$ alone.



5.1 Introduction



- □ Similarly, let $i_{c_k}(t)$ denote the current through Z due to the current source $i_k(t)$ acting alone, see Fig. 5.2c.
- By the superposition principle, the total current $i_T(t)$ due to all of the sources is equal to the algebraic sum, see Eq. 5.1.



5.2 System Elements

$$i_{_{T}} = \sum_{_{j=1}^{n} i_{v_{_{j}}}}^{n} + \sum_{_{k=1}^{m} i_{c_{_{k}}}}^{n}$$

(5.1)

 \Box Here, we will assume that the positive polarity for voltage is the tail of the current arrow, see Fig. 5.3. A recap of the voltage-current relations for *R*, *L* and *C*.



Fig. 5.4: (*a*) Capacitor; (*b*) Capacitor with initial voltage.

5.2 System Elements Cont'd



Fig. 5.5: (*a*) Inductor. (*b*) Inductor with initial current.

Resistor. The resistor relates voltage and current as follows, see Fig. 5.3.

$$v(t) = Ri(t)$$

$$i(t) = Gv(t) ; \text{ with } G = \frac{1}{R}$$
(5.2)

here R is given in ohms and G in mhos.

Capacitor. For the capacitor shown in Fig. 5.4*a* the *v*-*i* relationships are

$$i(t) = C \frac{dv(t)}{dt} \qquad v(t) = \frac{1}{C} \int_{0-}^{t} i(\tau) d\tau + v_{C}(0-)$$
(5.3)

where C is given in farads. The initial value $v_C(0-)$ is the voltage across the capacitor just before the switching action.

5.2 System Elements Cont'd

- □ Note that, $v_C(0-) = v_C(0+)$ for all excitations except impulses and their derivatives.
- □ **Inductor.** The inductor in Fig. 5.5a describes the dual relationship between voltage and current when compared to a capacitor. Thus,

$$v(t) = L \frac{di(t)}{dt} \qquad i(t) = \frac{1}{L} \int_{0-}^{t} v(\tau) d\tau + i_L(0-)$$
(5.4)

where L is in henrys. The initial current $i_L(0-)$ can be regarded as an independent current source, as shown in Fig. 5.5b.

□ Note once again that, $i_L(0-) = i_L(0+)$ for all excitations except for impulses and their derivatives.

5.2 System Elements Cont'd

- □ If system elements are interconnected, integrodifferential equations arise relating the excitation to the response.
- □ Kirchhoff's voltage and current laws will be exploited to formulate equations.
- □ Recall, if the number of branches in the circuit is *B*, and if the number of nodes is *N*, the number of independent loop equations for the circuit is B N + 1.

[Example 5.1] System Elements



- Ger For the system in Fig. 5.6,
- a) Determine the number of independent loop equations.
- b) Hence, formulate these loop equations.

[Example 5.1] System Elements Cont'd

[Solution]

- (a) Clearly the circuit of Fig. 5.6 has seven branches and five nodes. Thus, there are 7-5+1=3 independent mesh equations.
- (b) Noting that capacitors in the circuit have associated initial voltages, the mesh equations are:
- $G Mesh i_1$: KVL yields

$$v_{1}(t) - v_{C_{1}}(0-) = R_{1}i_{1}(t) + \frac{1}{C_{1}}\int_{0-}^{t}i_{1}(\tau)d\tau - \frac{1}{C_{1}}\int_{0-}^{t}i_{2}(\tau)d\tau$$
WL violds

Get Mesh i_2 : KVL yields

$$\begin{split} v_{C_1}(0-) - v_{C_2}(0-) &= -\frac{1}{C_1} \int_{0-}^t i_1(\tau) d\tau + L \frac{di_2(t)}{dt} \\ &+ \left\{ \frac{1}{C_1} + \frac{1}{C_2} \right\} \int_{0-}^t i_2(\tau) d\tau - \frac{1}{C_2} \int_{0-}^t i_3(\tau) d\tau \end{split}$$

[Example 5.1] System Elements Cont'd

Get Mesh i_3 : KVL yields

$$-v_{2}(t) + v_{C_{2}}(0-) = -\frac{1}{C_{2}} \int_{0-}^{t} i_{2}(\tau) d\tau + \frac{1}{C_{2}} \int_{0-}^{t} i_{3}(\tau) d\tau + R_{2}i_{3}(t)$$
(5.5)

Ger Upon determining i_1 , i_2 and i_3 , we can determine branch currents and voltages across the elements, for instance,

$$i_{C_1}(t) = i_1(t) - i_2(t)$$

$$i_{C_2}(t) = i_2(t) - i_3(t)$$
(5.6)

Ger If the voltage $v_3(t)$ in Fig. 5.6 is our objective, we see that

$$v_3(t) = i_3(t)R_2$$
 (5.7)

5.2 System Elements

□ Let us use KCL for nodal analysis of a system. If the number of nodes in the network is N, the number of independent node equations required is N - 1.



Fig. 5.7.

- Consider the network in Fig. 5.7.
 We write a set of node equations in the network with the datum node shown.
- □ Since the number of nodes in the network N = 3, we need
 - N-1=2 independent equations.



5.3 Initial and Final Conditions

- We consider some methods for obtaining initial conditions for circuit differential equations.
- Examine ways to obtain particular integrals for systems with constant (dc) or sinusoidal (ac) excitations.
- □ In the solution of system ODEs, the complementary function is called the transient solution or free response.
- The particular integral is known as the forced response. In the case of constant or periodic excitations, the forced response at $t = \infty$ is the steady-state or final solution.
- Initial conditions at t = 0 + for a system are gotten through the ODEs describing the system or through the knowledge of the physical behavior of the *R*, *L*, and *C* elements in the system.

5.3 Initial and Final Conditions Cont'd

☐ Initial conditions for a capacitor. For a capacitor, the *v*-*i* relationship at

$$t = 0 + is$$

$$v_{C}(0+) = \frac{1}{C} \int_{0-}^{0+} i(\tau) d\tau + v_{C}(0-)$$
(5.9)

□ If i(t) contains no impulses or their derivatives, $v_C(0+) = v_C(0-)$. If q is the charge on the capacitor at t = 0 -, the initial voltage is

$$v_{C}(0+) = v_{C}(0-) = \frac{q}{C}$$
(5.10)

At t = 0 +, we can replace the capacitor by a voltage source if the initial charge exist, or by a short circuit if there is no initial charge.

[Example 5.2] Initial and Final Conditions

Consider the *R*-*C* network in Fig. 5.8*a*. The switch is closed at t = 0, and we assume there is no initial charge in the capacitor. Let us find the initial conditions i(0+) and i'(0+) for the ODE of the circuit.

[Example 5.2] Initial and Final Conditions Cont'd



[Example 5.2] Initial and Final Conditions Cont'd

Ger To obtain i'(0+), we must refer to the ODE

$$V\delta(t) = Ri'(t) + \frac{i(t)}{C}$$
(5.13)

 $\operatorname{Ger} \operatorname{At} \quad t = 0 + \text{we have}$

$$0 = Ri'(0+) + \frac{i(0+)}{C}$$
(5.14)

G√We the obtain

$$U'(0+) = -\frac{i(0+)}{RC} = -\frac{V}{R^2C}$$
(5.15)

The final condition, or steady-state solution, for the current in Fig. 5.8*a* is obtained from our knowledge of dc circuits. For a dc excitation, a capacitor is an open circuit for dc current. Thus the steady-state current is

$$i_p(t) = i(\infty) = 0$$

5.3 Initial and Final Conditions

Initial conditions for an inductor. For an inductor, the v-*i* relationship at

t = 0 + is

$$i_{L}(0+) = \frac{1}{L} \int_{0-}^{0+} v(\tau) \, d\tau + i_{L}(0-)$$
(5.16)

(5.17)

- □ If v(t) contains no impulses or their derivatives, $i_L(0+) = i_L(0-)$. If there is no initial current, $i_L(0+) = 0$, which corresponds to an open circuit at t = 0 +.
- Note that the current through an inductor cannot change instantaneously due to the conservation of flux linkage.

[Example 5.3] Initial and Final Conditions

Gev In Fig. 5.9a, the switch closes at t = 0. Let us find the initial conditions i(0+) and i'(0+) for the differential equation

$$Vu(t) = L \frac{di(t)}{dt} + Ri(t)$$

[Example 5.3] Initial and Final Conditions Cont'd



[Example 5.3] Initial and Final Conditions Cont'd

The steady-state solution for the circuit in Fig. 5.9a is obtained through the knowledge that for a dc source, an inductor is a short circuit.

$$i_p(t) = i(\infty) = \frac{V}{R}$$

[Example 5.4] Initial and Final Conditions



For the system of Fig. 5.10 the switch is closed at t = 0. Use the equivalent circuit models at t = 0 + and $t = \infty$ to obtain the initial conditions and steadystate solutions.

(5.21)

[Example 5.4] Initial and Final Conditions Cont'd

[Solution]



5.3 Initial and Final Conditions Cont'd

□ Final conditions for sinusoidal excitations

- □ For a pure sinusoidal excitation, the steady-state currents and voltages in the circuit are also sinusoids of the same frequency as the excitation.
- If the unknown is a voltage, for example, $v_1(t)$, the steady-state solution would take the form of Eq. 5.24.

$$v_{1p}(t) = \left| V(j\omega_0) \right| \sin \left[\omega_0 t - \phi(\omega_0) \right]$$
(5.24)

where ω_0 is the frequency of the excitation, and $|V(j\omega_0)|$ and $\phi(\omega_0)$ are the magnitude and phase of $v_{1p}(t)$ respectively.

A similar expression would hold if the unknown were a current.



5.3 Initial and Final Conditions Cont'd

- □ Standard procedures in ac circuit analysis are exploited to obtain the magnitude and the phase. For example, consider the *R*-*C* circuit in Fig. 5.12.
- The current generator is



5.4 Step and Impulse Response



Fig. 5.13.

- □ If the excitation is a step voltage, the physical analogy is that of a switch-closing at time t = 0, which connects a 1 V battery to a circuit.
- The physical analogy of an impulse excitation is that of a very short pulse (compared to the time constants of the circuit) with large amplitude.

[Example 5.5] Step and Impulse Response

Ger For the series *R*-*C* circuit in Fig. 5.13 find the impulse response.

[Solution]

A The ODE of the circuit is

$$\mathcal{CA}$$
Assuming $v_{C}(0-) = 0$.

$$v(t) = \delta(t) = Ri(t) + \frac{1}{C} \int_{0-}^{t} i(\tau) d\tau$$

(5.29)



[Example 5.5] Step and Impulse Response Cont'd

Since Eq. 5.29 contains an integral, we substitute x'(t) for i(t) in the equation, which yields

$$\delta(t) = Rx'(t) + \frac{1}{C}x(t)$$
(5.30)

Ger Integrating both sides between 0 - and 0 + gives

$$x(0+) = \frac{1}{R}$$
(5.31)

Ger The characteristic equation is

$$H(p) = Rp + \frac{1}{C}$$
(5.32)

and with little effort we have

$$x(t) = \frac{1}{R} e^{-t/RC} u(t)$$
(5.33)

[Example 5.5] Step and Impulse Response Cont'd



We arrived at the current impulse response i(t) as the result of an impulse voltage excitation. In the process we obtained the step response x(t) in Fig. 5.14b.



[Example 5.6] Step and Impulse Response

Consider the parallel R-C circuit in Fig. 5.12. Let it be driven by a step current source $i(t) = I_0 u(t)$, where I_0 is a constant. Assuming zero initial conditions, determine the step response. [Solution] $I_0 u(t) = Gv(t) + C \frac{dv(t)}{dt}$ (5.35)Gerr The ODE is Ger Thus, we obtain the characteristic equation (5.36)H(p) = Cp + GGet The steady-state value of v(t) is $v_{p}(t) = \frac{I_{0}}{H(0)} = \frac{I_{0}}{G} = I_{0}R$ (5.37)Ger Thus the complete solution for the voltage step response is $v(t) = (Ke^{-t/RC} + I_0R)u(t)$ (5.38)

[Example 5.6] Step and Impulse Response Cont'd



5.4 Step and Impulse Response Cont'd

Suppose the excitation in Fig. 5.12 were a pulse shown in Fig. 5.16.







(5.41)

Then by the superposition and time-invariant postulates of linear systems, the response would be

$$v(t) = I_0 R \left[(1 - e^{-t/RC}) u(t) - (1 - e^{-(t-T)/RC}) u(t-T) \right]$$

(5.42)

5.5 Solution of System Equations

- □ System equations are made up of mesh, node, or mixed basis.
- The choice between mesh and node equations depends largely upon the unknown quantities.

[Example 5.7] Solution of System Equations



Get Or, in terms of the numerical values, we have

$$2e^{-0.5t}u(t) = i(t) + 2\int_{0-}^{t} i(\tau) d\tau$$
(5.44)

Get Differentiating both sides of Eq. 5.44, we obtain

$$2\delta(t) - e^{-0.5t}u(t) = \frac{di(t)}{dt} + 2i(t)$$
(5.45)

To obtain the initial condition i(0+), we must integrate Eq. 5.45 between the limits t = 0 - and t = 0 + to give i(0+) = 2. From the characteristic eq.

$$H(p) = p + 2 = 0$$
 (5.46)

Ger The complementary function is thus

$$i_C(t) = Ke^{-2t}$$
 (5.47)

Ger Assume the particular integral to be $i_p(t) = A e^{-0.5t}$, then we obtain

$$A = -\frac{1}{H(-0.5)} = -\frac{2}{3}$$
(5.48)

Get The complete solution is

$$i(t) = Ke^{-2t} - \frac{2}{3}e^{-0.5t}$$
(5.49)

Ger From the initial condition i(0+) = 2, we obtain the final solution,

$$i(t) = \left\{\frac{8}{3}e^{-2t} - \frac{2}{3}e^{-0.5t}\right\}u(t)$$
(5.50)

As noted earlier, in the solution of system ODEs, the complementary function is called the free response, where as the forced response is a particular integral, and in the case of constant or periodic excitation, the forced response at $t = \infty$ is the steady-state solution.

1 Note, the free response is a function of the system elements alone.

5.5 Solution of System Equations Cont'd

- □ Whereas, the forced response depends on both the system and excitation.
- □ If the roots of the characteristic equation H(p) all have negative or zero real parts, the free response is made up of only damped exponential and/or sinusoids. That is, given $p_1 = \sigma \pm j\omega$ the root of H(p), then $\operatorname{Re}(p_1) = \sigma \leq 0$.
- □ Note that if a characteristic eq. contains only roots whose real parts are zero or negative, and if the $j\omega$ axis roots are simple, then the network it describes is said to be stable; otherwise, it is unstable.

Example 5.8 Solution of System Equations



[Solution]

Ge We have already obtained the particular integral in Eq. 5.28. Now let us find the complementary function. The ODE on a node basis is

$$C\frac{dv}{dt} + Gv = I_0 \sin \omega t \, u(t) \tag{5.51}$$

Ger from which we obtain the characteristic equation as

$$H(p) = Cp + G \tag{5.52}$$

G√ so that

$$v_C(t) = K e^{-Gt/C}$$
(5.53)

A and the incomplete solution is

$$v(t) = K e^{-Gt/C} u(t) + \frac{I_0}{(G^2 + \omega^2 C^2)^{1/2}} \sin\left\{\omega t - \tan^{-1}\frac{\omega C}{G}\right\} u(t)$$
(5.54)

Ger From initial condition v(0-) = 0, we obtain

5.5 Solution of System Equations Cont'd



Fig. 5.21.

- Next, we examine an example of different kinds of free responses of a second-order system equation that depend on relative values of the system elements.
- □ Suppose we are given the system in Fig. 5.21; let us find the free response $v_C(t)$ for the ODE

(5.59)

(5.60)

$$i_{g}(t) = C \frac{dv}{dt} + Gv + \frac{1}{L} \int_{0-}^{t} v(\tau) d\tau + i_{L}(0-)$$
(5.58)

Differentiating both sides of Eq. 5.58, we have

$$i'_{g}(t) = Cv''(t) + Gv'(t) + \frac{1}{L}v(t)$$

The characteristic equation is then

$$H(p) = Cp^{2} + Gp + \frac{1}{L} = C\left\{p^{2} + \frac{G}{C}p + \frac{1}{LC}\right\}$$

5.5 Solution of System Equations Cont'd

In factored form,
$$H(p)$$
 is $H(p) = C(p - p_1)(p - p_2)$ (5.61)where $p_1 \\ p_2 \\ p_2 \\ end{tabular} = -\frac{G}{2C} \pm \frac{1}{2} \left[\left(\frac{G}{C} \right)^2 - \frac{4}{LC} \right]^{1/2} = -A \pm B$ (5.62)There are three different kinds of responses depending upon whether *B* is real, zero, or imaginary. $\left(\frac{G}{C} \right)^2 > \frac{4}{LC} \\ CASE 1. B is real, that is, \\ Then the free response is $v_c(t) = K_1 e^{-(A-B)t} + K_2 e^{-(A+B)t}$ (5.63) $k_1 + K_2 + K_2$$

Fig. 5.22. Overdamped response.

Department of Electrical & Electronic Engineering, School of Engineering, University of Zambia

t

0



□ When B = 0, the response is critically damped, as shown in Fig. 5.23.



5.5 Solution of System Equations Cont'd

CASE 3. *B* is imaginary, that is,

$$\left(\frac{G}{C}\right)^2 < \frac{4}{LC}$$

Letting $B = j\beta$, we have

$$v_{C}(t) = e^{-At} (K_{1} \sin \beta t + K_{2} \cos \beta t)$$
 (5.63)

□ Here, the response is said to be underdamped, and is shown by the damped oscillatory curve in Fig. 5.24.



- A look at simultaneous system equations. We once again rely upon physical reasoning rather than formal mathematical operations to obtain the initial currents and voltages as well as the steady-state solutions. In the system of Fig. 5.25, the switch *S* is thrown from position 1 to position 2 at t = 0. it is known that prior to t = 0, the circuit had been in steady state. We make the idealized assumption that the switch closes instantaneously at t = 0.
- Gev Our task is to find $i_1(t)$ and $i_2(t)$ after the switch position changes. The values of the batteries V_1 and V_2 are $V_1 = 2v$, $V_2 = 3v$; and the element values are given as



Given The mesh equations for $i_1(t)$ and $i_2(t)$ after t = 0 are

$$V_{2} = Li'_{1}(t) + R_{1}i_{1}(t) - R_{1}i_{2}(t)$$
(5.64)

$$-v_{C}(0-) = -R_{1}i_{1}(t) + \frac{1}{C}\int_{0-}^{t}i_{2}(\tau)d\tau + (R_{1}+R_{2})i_{2}(t)$$
(5.65)

Since Eq. 5.65 contains an integral, we differentiate it to give

$$0 = -R_1 i'_1(t) + \frac{1}{C} i_2(t) + (R_1 + R_2) i'_2(t)$$
(5.66)

Ge Using Eqs. 5.64 and 5.66 as our system of equations, we obtain the characteristic equation

$$H(p) = \begin{vmatrix} Lp + R_1 & -R_1 \\ -R_1p & \frac{1}{C} + (R_1 + R_2)p \end{vmatrix} = L(R_1 + R_2)p^2 + \left(\frac{L}{C} + R_1R_2\right)p + \frac{R_1}{C}$$
(5.67)

Get Substituting the element values into H(p), we have

$$H(p) = 2.5p^2 + 4p + 1.5 = 2.5(p+1)(p+0.6)$$
(5.68)

Get The free response are then

$$i_{1C}(t) = (K_1 e^{-0.6t} + K_2 e^{-t}) u(t)$$

$$i_{2C}(t) = (K_3 e^{-0.6t} + K_4 e^{-t}) u(t)$$
(5.69)

(5.70)

GeV The steady-state solutions for the mesh currents are obtained at $t = \infty$ by considering the circuit from a dc viewpoint. The inductor is then a short circuit and the capacitor is an open circuit; thus we have

$$i_{1p}(t) = \frac{V_2}{R_1} = 6 \text{ amp}$$

 $i_{2p}(t) = 0$

G√Now let us determine the initial currents and voltages, which incidentally, have the same values at t = 0 − and t = 0 + because the voltage sources are not impulses.
G√Before the switch is thrown at t = 0, the circuit with V₁ as the voltage source was at steady state. Consequently,

$$v_{C}(0-) = V_{1} = 2v; \quad i_{1}(0-) = \frac{V_{1}}{R_{1}} = 4 \text{ amp}; \quad i_{2}(0-) = 0$$
 (5.71)

Geo We next find $i'_1(0+)$ from Eq. 5.64 at t = 0 +.

$$V_{2} = Li'_{1}(0+) + R_{1}i_{1}(0+) - R_{1}i_{2}(0+)$$
(5.72)

Substituting numerical values into Eq. 5.74, we find $i'_1(0+) = 1 \text{ amp/sec}$

Ger From Eq. 5.68 at t = 0 +, we obtain similarly

$$i'_{2}(0+) = \frac{R_{1}}{R_{1} + R_{2}} i'_{1}(0+) = 0.2 \text{ amp/sec}$$
 (5.73)

Solutions With these initial values of $i_1(t)$ and $i_2(t)$, we can quickly arrive at the final solutions



5.6 Analysis of Transformers

□ By Faraday's law of induction, a current i_1 flowing in a coil L_1 may induce a current i_2 in a closed loop containing a second coil L_2 .



Fig. 5.27. Transformer.

- □ To induce the current i₂, (a) part of the flux
 Φ₁ in the coil L₁ must be coupled magnetically to the coil L₂, (b) the flux
 Φ₁ must be changing with time.
 □ Here we will analyze circuits having a
 - transformer. A schematic of a transformer is shown in Fig. 5.27.

The L_1 side is usually referred to as the primary coil and L_2 side called as the secondary coil. The energy source is generally at the primary. Mathematically the transformer in Fig. 5.27 is described as

$$v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}; \quad v_2(t) = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

(5.75)

□ Where *M* is the mutual inductance associated with the flux linking L_1 to L_2 , and is related to L_1 and L_2 by

(5.76)

$$M = K \sqrt{L_1 L_2}$$

■ Here *K* is called the coefficient of coupling. It is bounded by the limits $0 \le |K| \le 1$. If |K| = 1, then all of flux Φ_1 in coil L_1 is linked magnetically to L_2 .

- If K = 0, the coils may be regarded as two separate coils having no effect upon one another.
- □ For circuits with transformers, reference polarities for mutually induced voltages $M \frac{di}{dt}$, are given by small dots painted on the input and output leads of a transformer.
- □ If both currents $i_1(t)$ and $i_2(t)$ flow into the dots or away from the dots, $M \frac{di}{dt}$ is positive. If one current flows into the dot and the other away from the second dot, the sign of $M \frac{di}{dt}$ is negative.



If N₁ and N₂ are the number of turns of coils L₁ and L₂, then the flux linkages of L₁ and L₂ are given by N₁Φ₁ and N₂Φ₂, respectively.
 If both currents flow into the dots, sum of flux linkages is

$$\sum \Phi \text{ linkages} = N_1 \Phi_1 + N_2 \Phi_2 \tag{5.77}$$

□ If, however, one of the currents, for example, i_1 , flows into the dot, and the other i_2 flows out of the other dot, then

$$\sum \Phi \text{ linkages} = N_1 \Phi_1 - N_2 \Phi_2$$
 (5.78)

□ Note, the sum of flux linkages is continuous with time.

The differential equations for the transformer in Fig. 5.28 are

$$Vu(t) = L_1 i'_1(t) + R_1 i_1(t) + M i'_2(t)$$

$$0 = M i'_1(t) + R_2 i_2(t) + L_2 i'_2(t)$$

(5.79)



Integrating this set of equations between t = 0 - and t = 0 + results in the determinant

$$\begin{bmatrix} L_1 \begin{bmatrix} i_1(0+) - i_1(0-) \end{bmatrix} & M \begin{bmatrix} i_2(0+) - i_2(0-) \end{bmatrix} \\ M \begin{bmatrix} i_1(0+) - i_1(0-) \end{bmatrix} & L_2 \begin{bmatrix} i_2(0+) - i_2(0-) \end{bmatrix}$$
(5.80)

Evaluating the determinant we get

$$(L_1 L_2 - M^2) \left[i_1(0+) - i_1(0-) \right] \left[i_2(0+) - i_2(0-) \right] = 0$$
(5.81)

If $L_1L_2 > M^2$, that is, K < 1, then the currents must be continuous at t = 0 in order for the determinant in Eq. 5.82 to be equal to zero. Thus

$$i_1(0+) = i_1(0-), \quad K < 1$$
 (5.82)
 $i_2(0+) = i_2(0-), \quad K < 1$ (5.83)

and

[Example 5.9] Analysis of Transformers



For the transformer circuit in Fig. 5.28, $L_1 = 1h$, $L_2 = 2h$, $R_1 = 3\Omega$, $R_2 = 8\Omega$ and M = 1h. The excitation is V = 6u(t). Let us find $i_1(t)$ and $i_2(t)$, assuming that $i_1(0-) = i_2(0-) = 0$.

The differential equations for the circuit are

$$i'_{1}(t) + 3i_{1}(t) + i'_{2}(t) = 6u(t)$$

$$i'_{1}(t) + 2i'_{2}(t) + 8i_{2}(t) = 0$$
(5.84)

Ger The characteristic equation is given by the determinant

$$H(p) = \begin{vmatrix} p+3 & p \\ p & 2p+8 \end{vmatrix} = (p+3)(2p+8) - p^2 = (p^2 + 14p + 24)$$

= $(p+2)(p+12)$ (5.85)

[Example 5.9] Analysis of Transformers Cont'd

Grant Thus the complementary functions are

$$\vec{t}_{1c}(t) = K_1 e^{-2t} + K_2 e^{-12t}
\vec{t}_{2c}(t) = K_3 e^{-2t} + K_4 e^{-12t}$$
(5.86)

Ger To obtain the particular integral, or steady-state solution, we rely upon physical reasoning to arrive at

$$i_{1p}(t) = \frac{V}{R_1} = 2 \operatorname{amp}$$

 $i_{2p}(t) = 0 \operatorname{amp}$
(5.87)

Ger Since the excitation does not contain an impulse (and since $L_1L_2 - M^2 \neq 0$), we can assume that $i_1(0+)$ and $i_2(0+)$ are also zero. Then using Eq. 5.86 we can find $i'_1(0+)$ and $i'_2(0+)$.

$$i'_{1}(0+) + i'_{2}(0+) = 6$$

$$i'_{1}(0+) + 2i'_{2}(0+) = 0$$
(5.88)

[Example 5.9] Analysis of Transformers Cont'd

Solving, we find $i'_1(0+) = 12$ and $i'_2(0+) = 6$. With these initial conditions, we obtain the final solutions of $i_1(t)$ and $i_2(t)$.

$$i_{1}(t) = \left(2 - \frac{6}{5}e^{-2t} - \frac{4}{5}e^{-12t}\right)u(t); \quad i_{2}(t) = \left(-\frac{3}{5}e^{-2t} + \frac{3}{5}e^{-12t}\right)u(t)$$
(5.89)

5.6 Analysis of Transformers Cont'd

□ Suppose, now, $L_1L_2 = M^2$, that is, K = 1, then $i_1(t)$ and $i_2(t)$ need not be continuous at t = 0. In fact, we will show that the currents are discontinuous at t = 0 for a unity-coupled transformer.

Assuming that K = 1, consider the mesh eq for the secondary at t = 0 + 1

$$R_{2}i_{2}(0+) = -Mi'_{1}(0+) - L_{2}i'_{2}(0+)$$

$$= -\frac{M}{L_{1}} \Big[L_{1}i'_{1}(0+) + Mi'_{2}(0+) \Big]$$
(5.90)
(5.91)

The mesh equation of the primary side then becomes

$$V = R_1 i_1(0+) + \left[L_1 i_1'(0+) + M i_2'(0+) \right] = R_1 i_1(0+) - \frac{L_1}{M} R_2 i_2(0+)$$
(5.92)

■ We need an additional equation to solve for $i_1(0+)$ and $i_2(0+)$. This is provided by the equation

$$L_{1}\left[i_{1}(0+)-i_{1}(0-)\right] - M\left[i_{2}(0+)-i_{2}(0-)\right] = 0$$
(5.93)

☐ Which is obtained from Eq. 5.80. Since $i_1(0-) = i_2(0-) = 0$, we solve Eqs. 5.92 and 5.93 directly to give

$$\begin{split} i_1(0+) &= \frac{VL_2}{R_1L_2 + R_2L_1} \\ i_2(0+) &= \frac{-VM}{R_1L_2 + R_2L_1} \end{split}$$

(5.94)

Consider the following example. For the transformer in Fig. 5.28 the element values are

$L_1 = 4h,$	$L_{_2} = 1 h$
$R_1 = 8 \Omega,$	$R_{_2} = 3 \Omega$
M = 2h,	$V = 10 \mathrm{v}$

Assuming that the circuit is at steady-state before the switch is closed at t = 0, let us find $i_1(t)$ and $i_2(t)$. The DEs written on mesh basis are

$$\begin{aligned} &4\frac{di_{1}}{dt} + 8i_{1} + 2\frac{di_{2}}{dt} = 10\\ &2\frac{di_{1}}{dt} + \frac{di_{2}}{dt} + 3i_{2} = 0 \end{aligned}$$

(5.95)

(5.96)

The characteristic equation is

$$H(p) = \begin{vmatrix} 4(p+2) & 2p \\ 2p & (p+3) \end{vmatrix} = 0$$

which yields

$$H(p) = 20p + 24 = 20\left(p + \frac{6}{5}\right)$$

The complementary functions are

$$i_{1C}(t) = K_1 e^{-1.2t}$$

$$i_{2C}(t) = K_2 e^{-1.2t}$$
(5.98)

The particular integrals that we obtain by inspection are

$$i_{1p}(t) = \frac{V}{R_1} = \frac{10}{8} = \frac{5}{4}; \qquad i_{2p}(t) = 0$$
 (5.99)

The initial conditions are

$$i_{1}(0+) = \frac{VL_{2}}{R_{1}L_{2} + R_{2}L_{1}} = \frac{10}{20} = 0.5$$
$$i_{2}(0+) = \frac{-VM}{R_{1}L_{2} + R_{2}L_{1}} = -1.0$$

(5.100)

(5.97)

■ We thus find $K_1 = -0.75$ and $K_2 = -1.0$, so that

$$i_{1}(t) = (-0.75e^{-1.2t} + 1.25) u(t)$$

$$i_{2}(t) = -e^{-1.2t}u(t)$$
(5.101)

□ Notice that as t approaches infinity $i_2(t) \rightarrow 0$, while $i_1(t)$ goes to its steady-state value of 1.25.



End of Lecture 5

Thank you for your attention!