



# THE UNIVERSITY OF ZAMBIA

## SCHOOL OF ENGINEERING

### DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

#### UNIVERSITY EXAMINATIONS

FINAL EXAM – June / July 2015

**EEE 3112**

### **ELECTRICAL ENGINEERING PRACTICE**

---


<b>TIME</b>	: Three (3) hours
<b>INSTRUCTIONS</b>	: Answer any four (4) questions in section A and one question in section B.
<b>ADDITIONAL INFORMATION</b>	: 1. <b>Submit SECTION A and SECTION B in Separate Answer Booklets.</b>

---

**SECTION A: ANSWER AT LEAST Four (4) QUESTIONS FROM THIS SECTION**

**QUESTION 1**

- a) Briefly describe, giving two examples, what a standard is, and give the reason why we need to preserve it. **[3 Marks]**
- b) Give four categories of standards with their specific functions. **[2 marks]**
- c) Design an Aryton shunt to provide an ammeter with a current range of 0-1 mA, 5 mA, 10 mA and 20 mA. A D'Arsonval movement with an internal resistance of  $60\text{k}\Omega$  and full scale current of  $50\text{ }\mu\text{A}$  is used. **[13 Marks]**

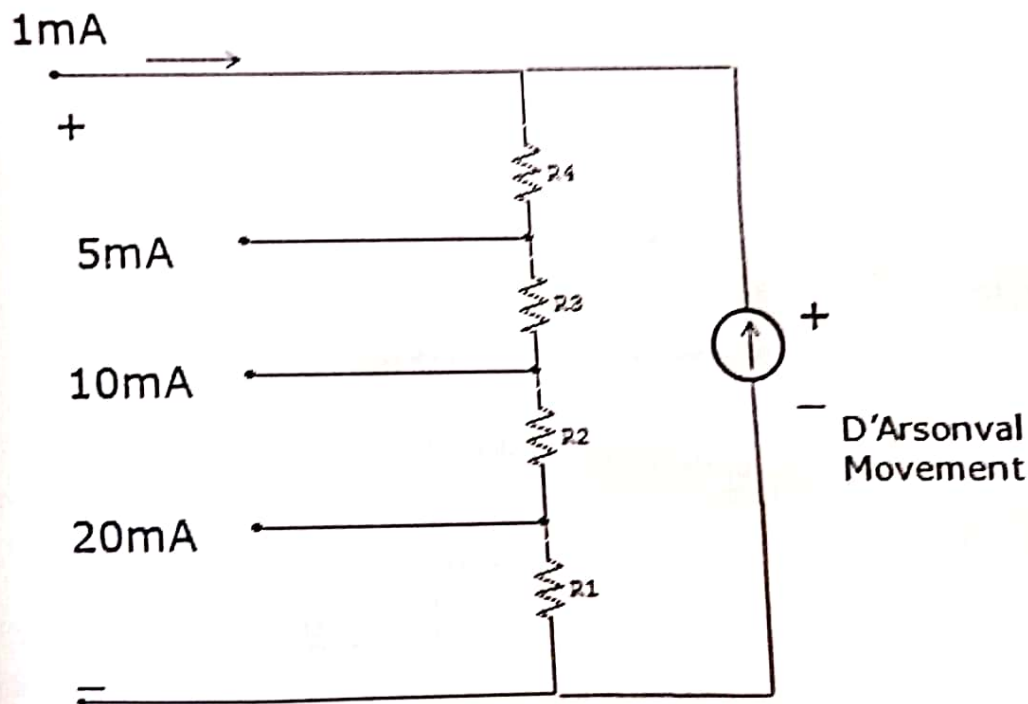

**Figure Q1 Aryton Shunt**



## Question 2

- a) Name any four classes of measuring instruments, giving one example for each. [2 Marks]
- b) Describe briefly four performance characteristics of an instrument. [4 marks]
- c) Outline four methods of fault finding. [4 Marks]
- d) A  $50\mu\text{A}$  full scale deflection current meter movement shown in figure Q5 is to be used in an Ohmmeter. The meter movement has an internal resistance  $R_m = 2\text{k}\Omega$  and a 3V battery is used in the circuit. Determine  $R_2$  at full scale deflection. [3 Marks]
- e) A  $100\Omega$  basic movement is to be used as an ohmmeter requiring a full scale deflection of 1mA and internal battery voltage of 5V. A half scale deflection marking of 2k is desired. Calculate: [4 Marks]
- value of  $R_1$  and  $R_2$
  - the maximum value of  $R_2$  to compensate for a 3% drop in battery voltage [3 Marks]

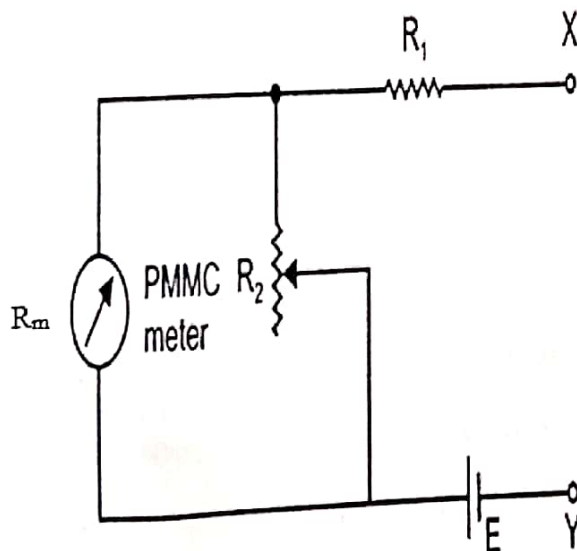


Figure Q5. Ohm meter

## Question 3

1. A student in a laboratory was presented with three resistors and two capacitor having the following colour bands and other characteristics:
- **Resistor 1:** Red, Green, Silver and Gold;

- **Resistor 2:** Violet, Grey, Gold and Silver;
  - **Resistor 3:** Yellow, Black, Red and White;
  - **Capacitor 1:** Red, Black and Orange;
  - **Capacitor 2:** Small capacitor with number code printed on it, 472K.
- i) Determine the resistance, capacitance and tolerance values of the above listed components. [5 Marks]
  - ii) State at least two functions of capacitors and one of resistors in electronic engineering. [3 Marks]
  - iii) Describe briefly the four main types of diagrams used in electrical and electronic engineering [4 Marks]
  - iv) Design and draw a circuit diagram of a simple 5 V regulated power supplier system and explain the functions of the devices (components) used. [6 Marks]
  - v) Calculate for the power rating of a  $480\ \Omega$  resistor with 10 V across it. [2 Marks]
- Total [20 Marks]**

#### Question 4

1. Figure 1 below shows a circuit diagram of a solar lamp. In the design three parallel high power white LEDs, each 2.7 V and 30 mA, are switched on in the evening and stay on for 10 hours using a 6 V 4.5 Ah rechargeable battery. During the day, the solar panel charges the battery as the white LEDs are switched off.

i) What are the functions of the following components:

- (1) 12 V solar panel;
  - (2) 6 V 100  $\Omega$  PCB Relay;
  - (3) Charger controller resistor connected in series with a silicon diode D1 (0.7 V);
  - (4) 1.8 V, 15 mA Red LED,
  - (5) High value 4700  $\mu\text{F}$  capacitor C1
- [1x5 Marks]**



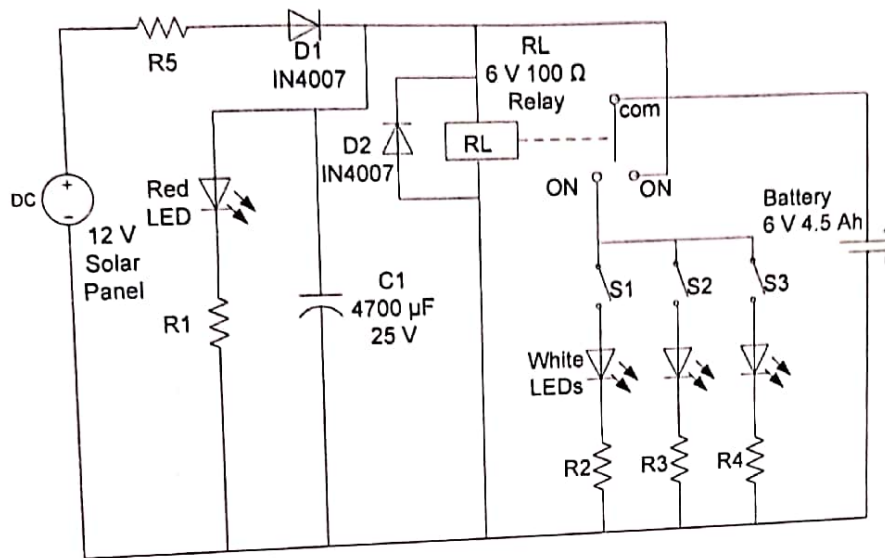



Figure 1: Solar lamp circuit diagram

- ii) Calculate the size of resistors R2, R3 and R4 needed to be connected in series with the white LEDs. [2 Marks]
- iii) Determine the size of resistor required to be connected in series with Red LED. [2 Marks]
- iv) What size of solar panel power is needed to charge the batter for a period of 5hours after been used for 10 hours (Assume that the battery was initially fully charged before use). [6 Marks]
- v) Briefly describe five main uses of electronic circuit diagrams. [5 Marks]

**Total [20 Marks]**

### Question 5

1. Draw a block diagram of a radio receiver system and explain the main functions of the components in it. [6 Marks]
2. What are the three main differences between average (mean) and rms values of a time varying current on an interval? Define form factor. [4 Marks]
3. Determine the colour bands for a  $1.5 \Omega \pm 5\%$  resistor. [2 Marks]
4. State the three uses of capacitor banks and one use of recloses in electrical power system. [4 Marks]
5. Figure 2, below, shows a solar charger monitor circuit diagram. Identify the components making up the circuit and make a bill of quantity. [4 Marks]

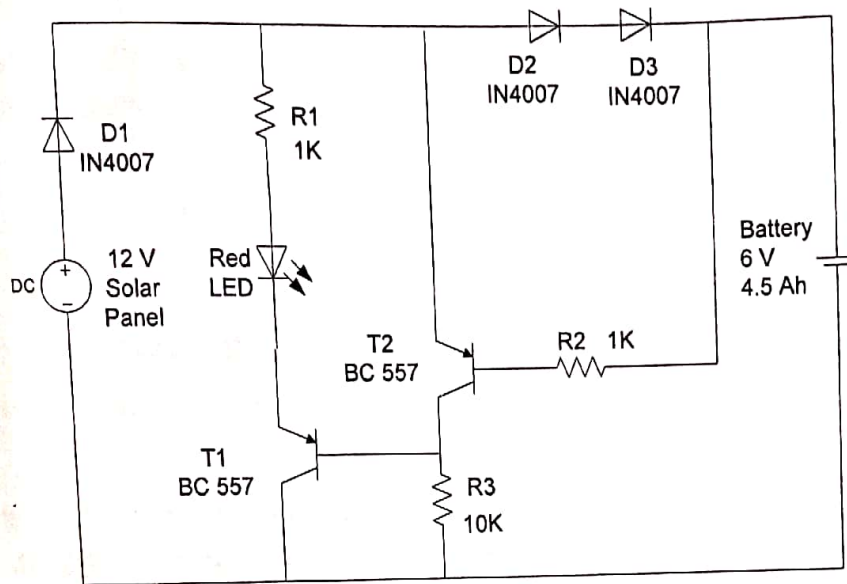

**Figure 2: Solar charger monitor circuit diagram.**

**Total [20 Marks]**

**SECTION B: ANSWER AT LEAST ONE (1) QUESTION FROM THIS SECTION**

**Question 6**

- (a) In a stone crusher at Chilanga Cement a steel shaft of 4m long, having a diameter of 60mm, is used to transmit power at a rotational speed of 600rev/min. If the maximum shear stress for the material of the shaft is limited to 75MN/m<sup>2</sup>. Determine the following
- (i) The maximum power that can be transmitted

- (ii) The corresponding angle of twist

Assume the modulus of rigidity for steel is  $95 \text{ GN/m}^2$ .

- (b) Define the modulus of rigidity,  $G$ .

[16+4=20 Marks]

### Question 7

- (a) The mass of a gear  $A$  in **Figure Q8 (a)**, is  $20 \text{ kg}$  and its centroidal radius of gyration,  $k_A$  is  $160 \text{ mm}$ . The mass of gear  $B$  is  $8 \text{ Kg}$  and its centroidal radius of gyration  $k_B$  is  $100 \text{ mm}$ .

- (i) Determine the mass moments of inertia of the two gears
- (ii) Write the differential equation of motion of the entire system given that the bearings have friction coefficients  $C_A = 0.05 \text{ Nm.s/rad}$  and  $C_B = 0.07 \text{ Nm.s/rad}$
- (iii) Calculate the angular acceleration of gear  $B$  when a torque of  $16 \text{ N.m}$  is applied to the shaft of gear  $A$ . Neglect friction.

- (iv) What is backlash in gearing systems

- (b) Define vibration resonance in forced vibration

[16+4=20 Marks]

END OF EEE3112 – Electrical Engineering Practice